

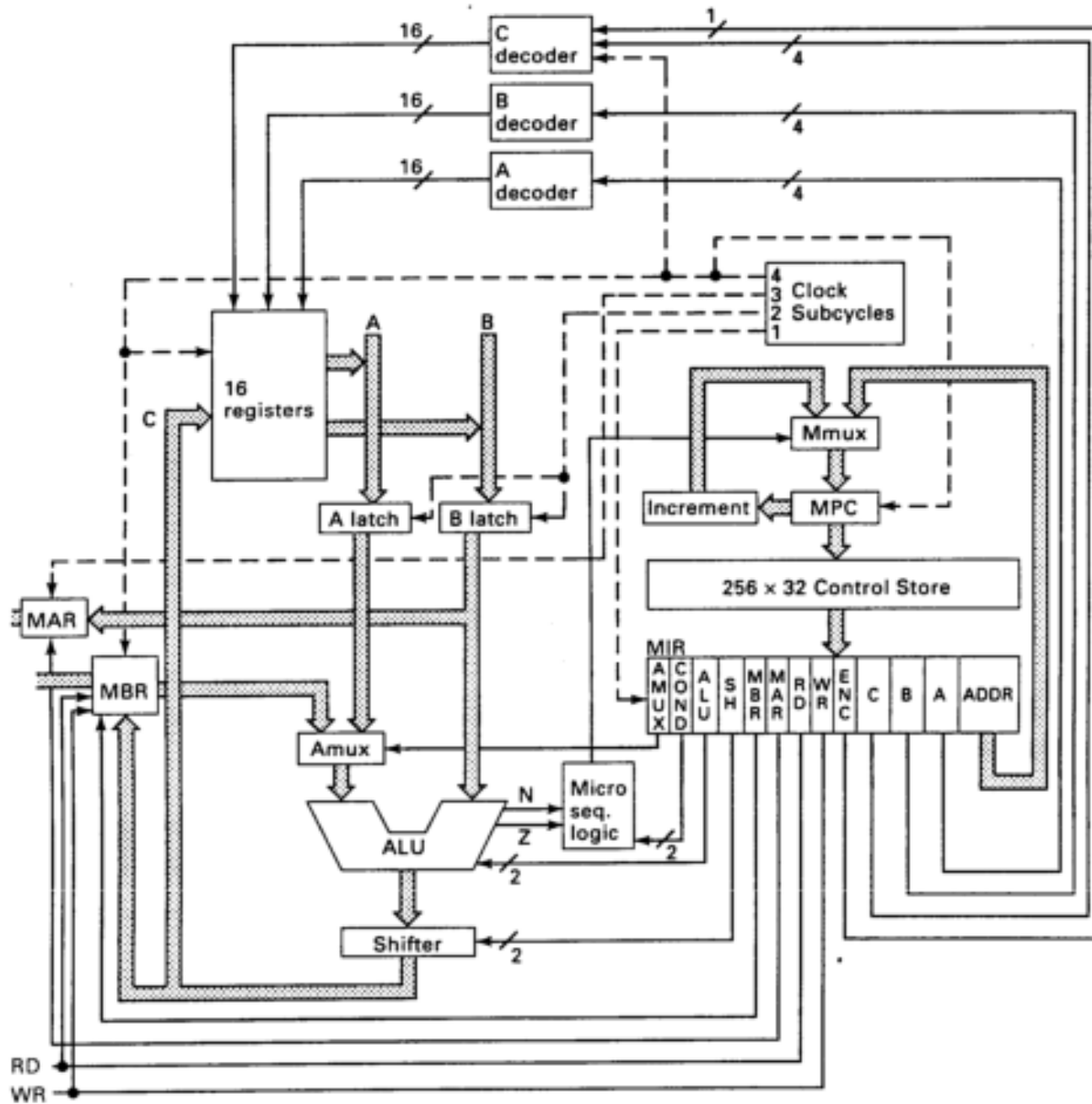


Teaching and Designing Microarchitecture in Racket

Jay McCarthy
UMass Lowell & PLT

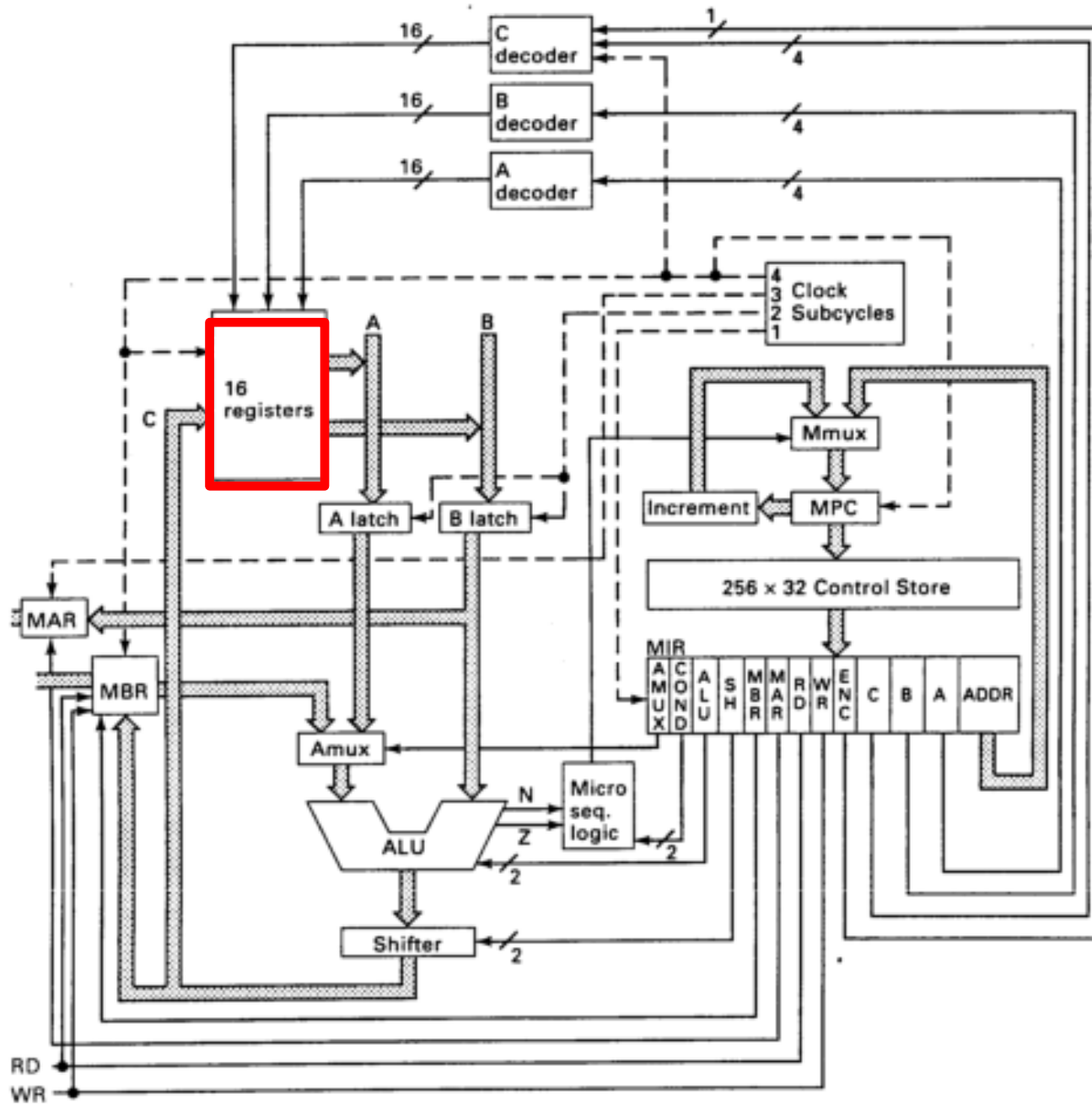

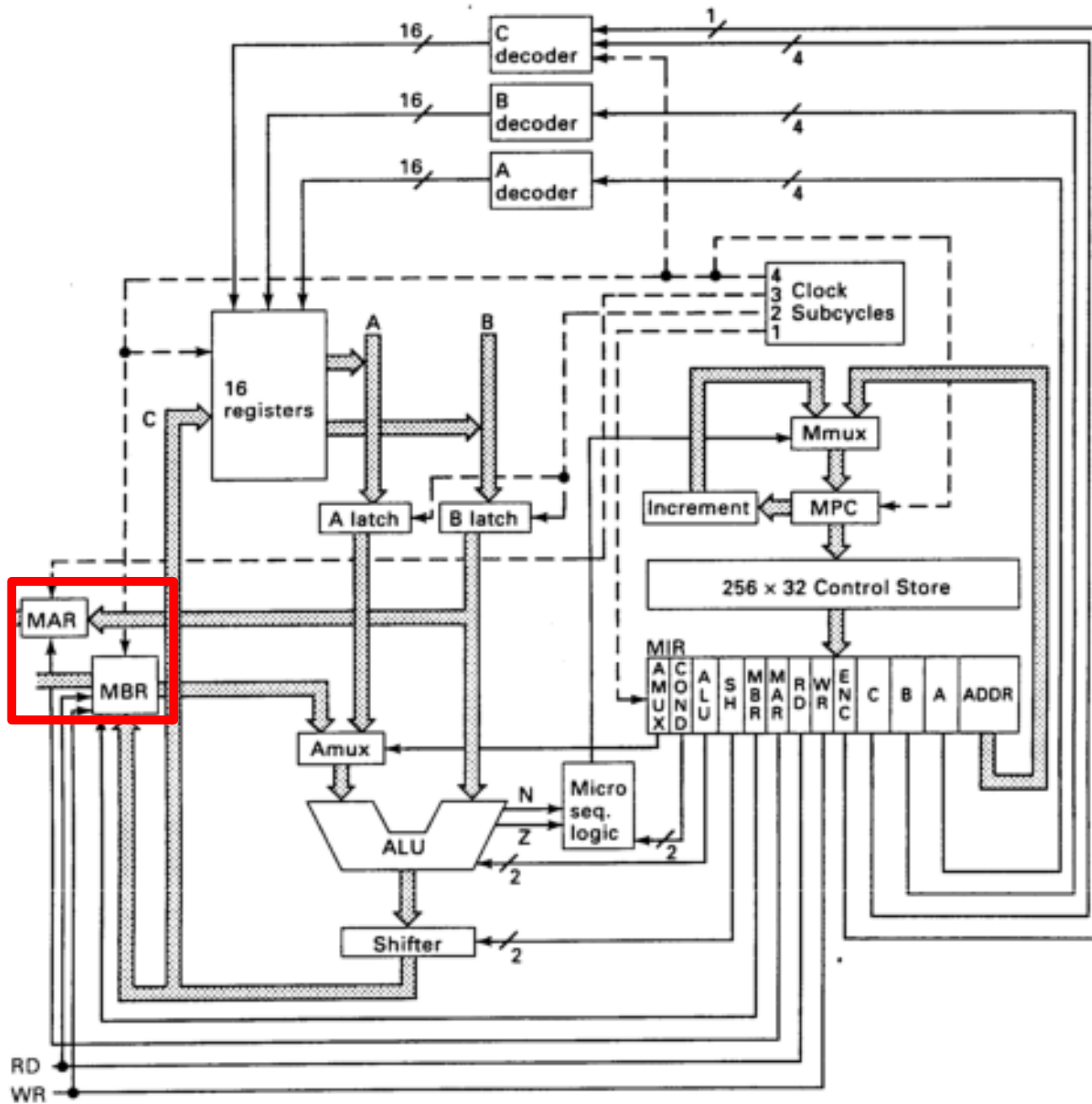



Binary	Mnemonic	Instruction	Meaning
0000xxxxxxxxxxxx	LODD	Load direct	$ac := m[x]$
0001xxxxxxxxxxxx	STOD	Store direct	$m[x] := ac$
0010xxxxxxxxxxxx	ADDD	Add direct	$ac := ac + m[x]$
0011xxxxxxxxxxxx	SUBD	Subtract direct	$ac := ac - m[x]$
0100xxxxxxxxxxxx	JPOS	Jump positive	if $ac \geq 0$ then $pc := x$
0101xxxxxxxxxxxx	JZER	Jump zero	if $ac = 0$ then $pc := x$
0110xxxxxxxxxxxx	JUMP	Jump	$pc := x$
0111xxxxxxxxxxxx	LOCO	Load constant	$ac := x$ ($0 \leq x \leq 4095$)
1000xxxxxxxxxxxx	LODL	Load local	$ac := m[sp + x]$
1001xxxxxxxxxxxx	STOL	Store local	$m[x + sp] := ac$
1010xxxxxxxxxxxx	ADDL	Add local	$ac := ac + m[sp + x]$
1011xxxxxxxxxxxx	SUBL	Subtract local	$ac := ac - m[sp + x]$
1100xxxxxxxxxxxx	JNEG	Jump negative	if $ac < 0$ then $pc := x$
1101xxxxxxxxxxxx	JNZE	Jump nonzero	if $ac \neq 0$ then $pc := x$
1110xxxxxxxxxxxx	CALL	Call procedure	$sp := sp - 1; m[sp] := pc; pc := x$
1111000000000000	PSHI	Push indirect	$sp := sp - 1; m[sp] := m[ac]$
1111001000000000	POPI	Pop indirect	$m[ac] := m[sp]; sp := sp + 1$
1111010000000000	PUSH	Push onto stack	$sp := sp - 1; m[sp] := ac$
1111011000000000	POP	Pop from stack	$ac := m[sp]; sp := sp + 1$
1111100000000000	RETN	Return	$pc := m[sp]; sp := sp + 1$
1111101000000000	SWAP	Swap ac, sp	$tmp := ac; ac := sp; sp := tmp$
11111100yyyyyyyy	INSP	Increment sp	$sp := sp + y$ ($0 \leq y \leq 255$)
11111110yyyyyyyy	DESP	Decrement sp	$sp := sp - y$ ($0 \leq y \leq 255$)

xxxxxxxxxxxx is a 12-bit machine address; in column 4 it is called x .
 yyyyyyy is an 8-bit constant; in column 4 it is called y .



Binary	Mnemonic	Instruction	Meaning
0000xxxxxxxxxxxx	LODD	Load direct	$ac := m[x]$
0001xxxxxxxxxxxx	STOD	Store direct	$m[x] := ac$
0010xxxxxxxxxxxx	ADDD	Add direct	$ac := ac + m[x]$
0011xxxxxxxxxxxx	SUBD	Subtract direct	$ac := ac - m[x]$
0100xxxxxxxxxxxx	JPOS	Jump positive	if $ac \geq 0$ then $pc := x$
0101xxxxxxxxxxxx	JZER	Jump zero	if $ac = 0$ then $pc := x$
0110xxxxxxxxxxxx	JUMP	Jump	$pc := x$
0111xxxxxxxxxxxx	LOCO	Load constant	$ac := x$ ($0 \leq x \leq 4095$)
1000xxxxxxxxxxxx	LODL	Load local	$ac := m[sp + x]$
1001xxxxxxxxxxxx	STOL	Store local	$m[x + sp] := ac$
1010xxxxxxxxxxxx	ADDL	Add local	$ac := ac + m[sp + x]$
1011xxxxxxxxxxxx	SUBL	Subtract local	$ac := ac - m[sp + x]$
1100xxxxxxxxxxxx	JNEG	Jump negative	if $ac < 0$ then $pc := x$
1101xxxxxxxxxxxx	JNZE	Jump nonzero	if $ac \neq 0$ then $pc := x$
1110xxxxxxxxxxxx	CALL	Call procedure	$sp := sp - 1; m[sp] := pc; pc := x$
1111000000000000	PSHI	Push indirect	$sp := sp - 1; m[sp] := m[ac]$
1111001000000000	POPI	Pop indirect	$m[ac] := m[sp]; sp := sp + 1$
1111010000000000	PUSH	Push onto stack	$sp := sp - 1; m[sp] := ac$
1111011000000000	POP	Pop from stack	$ac := m[sp]; sp := sp + 1$
1111100000000000	RETN	Return	$pc := m[sp]; sp := sp + 1$
1111101000000000	SWAP	Swap ac, sp	$tmp := ac; ac := sp; sp := tmp$
11111100yyyyyyyy	INSP	Increment sp	$sp := sp + y$ ($0 \leq y \leq 255$)
11111110yyyyyyyy	DESP	Decrement sp	$sp := sp - y$ ($0 \leq y \leq 255$)

xxxxxxxxxxxx is a 12-bit machine address; in column 4 it is called x .
 yyyyyyy is an 8-bit constant; in column 4 it is called y .



```

    STOL 0      ; AC = 0 => M[SP] = Fib(0)
    LOCO 1      ; True => AC = 1
    STOL 1      ; AC = 1 => M[SP+1] = Fib(1)
loop: ADDL 0    ; AC = Fib(n+1), M[SP] = Fib(n) => AC = Fib(n+2)
    STOL 2      ; AC = Fib(n+2) => M[SP+2] = Fib(n+2)
    INSP 1      ; increment n & SP
    JPOS loop:  ; If Fib(n+2) was negative, then n = 24

```

=>

```

100100000000000000
011100000000000001
100100000000000001
101000000000000000
100100000000000010
111111000000000001
010000000000000011

```





```

(grammar
  (Program [() empty]
    [(Inst Program) (cons $1 $2)])
  (Arg [(NUM) $1] [(LABEL) (as-lref $1)])
  (Inst [(LABEL) (as-ldef $1)]
    [( NUM) (as-lnum $1)]
    [( STR) (as-lstr $1)]
    [( LOC NUM) (as-rloc $2)]
    [(LODD Arg) (as-iarg "0000" $2)]
    [(STOD Arg) (as-iarg "0001" $2)]
    [(ADDD Arg) (as-iarg "0010" $2)]
    [(SUBD Arg) (as-iarg "0011" $2)]
    [(JPOS Arg) (as-iarg "0100" $2)]
    [(JZER Arg) (as-iarg "0101" $2)]
    [(JUMP Arg) (as-iarg "0110" $2)]
    [(LOCO Arg) (as-iarg "0111" $2)]
    [(LODL Arg) (as-iarg "1000" $2)]
    [(STOL Arg) (as-iarg "1001" $2)]
    [(ADDL Arg) (as-iarg "1010" $2)]
    [(SUBL Arg) (as-iarg "1011" $2)]
    [(JNEG Arg) (as-iarg "1100" $2)]
    [(JNZE Arg) (as-iarg "1101" $2)]
    [(CALL Arg) (as-iarg "1110" $2)]
    [(PSHI) (as-inst "1111000000000000")]
    [(POPI) (as-inst "1111001000000000")]
    [(PUSH) (as-inst "1111010000000000")]
    [( POP) (as-inst "1111011000000000")]
    [(RETN) (as-inst "1111100000000000")]
    [(SWAP) (as-inst "1111101000000000")]
    [(INSP Arg) (as-iarg "11111100" $2)]
    [(DESP Arg) (as-iarg "11111110" $2)]
    [(HALT) (as-inst "1111111100000000")]))

```



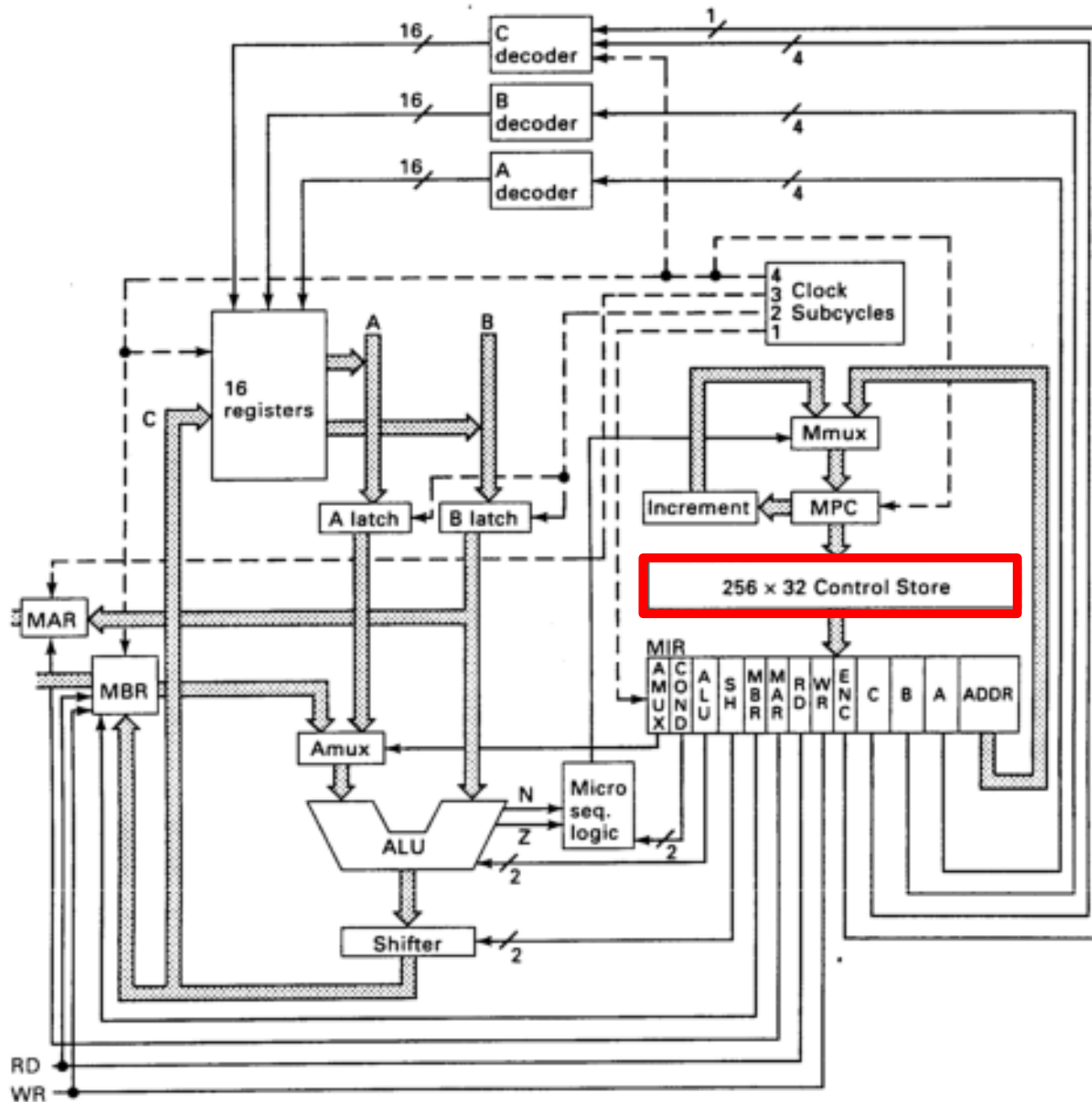

 

<u>AMUX</u>	<u>COND</u>	<u>ALU</u>	<u>SH</u>	<u>MBR, MAR, RD, WR,</u>
0 = A latch 1 = MBR	0 = No jump 1 = Jump if N = 1 2 = Jump if Z = 1 3 = Jump always	0 = A + B 1 = A AND B 2 = \bar{A} 3 = \bar{A}	0 = No shift 1 = Shift right 1 bit 2 = Shift left 1 bit 3 = (not used)	0 = No 1 = Yes



00000000101111010010011000000000
00000000001111110110011000000000
00010001101110111101011000000000
00000000001111101111011000000000
00000000000110101010101100000000
00000000000111011111001000000000
00110001101000001101101000001011
00000000001100100010111000000000
00000000000110111011101000000000
00110001101000000010101100001011
01110000001100100000110100000100
01100000011000000000000000000000



START:

mar := sp; d := (1) + sp; wr;

f := (1) + (1); wr;

mbr := (1); b := (1); mar := d; wr;

e := f + (1); wr;

LOOP:

a := a + b;

d := f + sp;

mar := d; mbr := a; wr; if n then goto DONE;

sp := sp + e; wr;

b := b + a;

mar := sp; mbr := b; wr; if n then goto DONE;

sp := d; goto LOOP; wr;

DONE:

wr; rd; goto START;



```

(define (µcompile-reg L reg which)
  (hash-set1 L reg
    (match which
      ["pc" 'PC] ["ac" 'AC] ["sp" 'SP] ["ir" 'IR] ["tir" 'TIR]
      ["0" 'Z] ["1" 'P1] ["(-1)" 'N1] ["amask" 'AMASK] ["smask" 'SMASK]
      ["a" 'A] ["b" 'B] ["c" 'C] ["d" 'D] ["e" 'E] ["f" 'F])))

(define (µcompile-b-bus L b-bus)
  (µcompile-reg L 'B b-bus))
(define (µcompile-c-bus L c-bus)
  (µcompile-reg L 'C c-bus))
(define (µcompile-a-bus L a-bus)
  (match a-bus
    ['mbr
     (hash-set1 L 'AMUX 'MBR)]
    [_
     (µcompile-reg L 'A a-bus)])))

(define (µcompile-alu L alu)
  (match alu
    [(alu-plus a-bus b-bus)
     (hash-set1 (µcompile-b-bus (µcompile-a-bus L a-bus) b-bus) 'ALU '+)]
    [(alu-id a-bus)
     (hash-set1 (µcompile-a-bus L a-bus) 'ALU 'A)]
    [(alu-band a-bus b-bus)
     (hash-set1 (µcompile-b-bus (µcompile-a-bus L a-bus) b-bus) 'ALU '&)]
    [(alu-inv a-bus)
     (hash-set1 (µcompile-a-bus L a-bus) 'ALU '!)])))

(define (µcompile-sh L sh)
  (match-define (sh-op alu) sh)
  (hash-set1
    (µcompile-alu L alu) 'SH
    (match sh
      [(sh-id _) 'NS]
      [(sh-lshift _) 'LS]
      [(sh-rshift _) 'RS])))

(define (µcompile-comp label->idx L comp)
  (match comp
    [(mc-setc c-bus sh)
     (hash-set1 (µcompile-c-bus (µcompile-sh L sh) c-bus) 'ENC 'ENC)]
    [(mc-alu alu)
     (µcompile-alu L alu)]
    [(mc-mar b-bus)
     (hash-set1 (µcompile-b-bus L b-bus) 'MAR 'MAR)]
    [(mc-mbr sh)
     (hash-set1 (µcompile-sh L sh) 'MBR 'MBR)]
    [(mc-if cond label)
     (hash-set1
       (hash-set1 L 'COND cond)
       'ADDR
       (hash-ref label->idx label
         (λ ()
           (error 'µcompile "L~a: Unknown label: ~v"
             (µcompile-line) label)))))]
    [(mc-rd) (hash-set1 L 'RD 'RD)]
    [(mc-wr) (hash-set1 L 'WR 'WR)]))

```




```

; ALU : N N 2 -> N 1 1
(define (ALU A B Function-Select #;=> Out Negative? Zero?)
  (define N (length A))
  (Net ([TheSum N] [TheAnd N] [NotA N] [Function-Selects 4]))
  (Adder/N A B FALSE #;=> GROUND TheSum)
  (And/N A B #;=> TheAnd)
  (Not/N A #;=> NotA)
  (Decoder/N Function-Select #;=> Function-Selects)
  (RegisterRead (list TheSum TheAnd A NotA) Function-Selects
    #;=> Out)
  (IsZero? Out #;=> Zero?)
  (IsNegative? Out #;=> Negative?)))

```




```

(define-chk-num chk-alu
  #:N N
  #:in ([A N] [B N] [Function-Select 2])
  #:out ([Out N] Negative? Zero?)
  #:circuit ALU #:exhaust 5
  #:check
  (chk (vector Out Negative? Zero?)
    (let* ([Ans-premod
            (match Function-Select
              [0 (+ A B)]
              [1 (bitwise-and A B)]
              [2 A]
              [3 (bitwise-not A)])])
      [Ans
       (modulo Ans-premod (expt 2 N))])
    (vector Ans
      (negative? (unsigned->signed N Ans))
      (zero? Ans))))))

```



```

(define (MIC1 µCodeLength Microcode
  Registers MPC-out
  Read? Write?
  MAR MBR)
  (define µAddrSpace (ROM-AddrSpace Microcode))
  (define WordBits (length MBR))
  (define RegisterCount (length Registers))
  (define RegisterBits (integer-length (sub1 RegisterCount)))
  (define MIR:RD Read?)
  (define MIR:WR Write?)
  (define-wires
    Clock:1 Clock:2 Clock:3 Clock:4
    N Z MicroSeqLogic-out
    [pre-MIR µCodeLength] [MIR µCodeLength]
    MIR:AMUX [MIR:COND 2] [MIR:ALU 2] [MIR:SH 2]
    MIR:MBR MBR? MIR:MAR MAR?
    MIR:ENC
    [MIR:C RegisterBits] [MIR:B RegisterBits] [MIR:A RegisterBits]
    [MIR:ADDR µAddrSpace]
    [Mmux-out µAddrSpace]
    MPC-Inc-carry [MPC-Inc-out µAddrSpace]
    [Asel RegisterCount] [Bsel RegisterCount] [Csel RegisterCount]
    [A-Bus WordBits] [B-Bus WordBits] [C-Bus WordBits]
    [A-latch-out WordBits] [B-latch-out WordBits]
    [Amux-out WordBits] [ALU-out WordBits]
    Shifter-Left? Shifter-Right? Write-C?)
  (Net ()
    (Clock (list Clock:1 Clock:2 Clock:3 Clock:4))
    (ROM Microcode MPC-out pre-MIR)
    (Latch/N Clock:1 pre-MIR MIR)
    (Cut/N MIR
      (reverse
        (list MIR:AMUX MIR:COND MIR:ALU MIR:SH
          MIR:MBR MIR:MAR MIR:RD MIR:WR
          MIR:ENC MIR:C MIR:B MIR:A MIR:ADDR)))
    (Decoder/N MIR:A Asel)
    (Decoder/N MIR:B Bsel)
    (Decoder/N MIR:C Csel)
    (RegisterRead Registers Asel A-Bus)
    (RegisterRead Registers Bsel B-Bus)
    (Latch/N Clock:2 A-Bus A-latch-out)
    (Latch/N Clock:2 B-Bus B-latch-out)
    (And MIR:MAR Clock:3 MAR?)
    (Latch/N MAR? B-latch-out MAR)
    (Mux/N A-latch-out MBR MIR:AMUX Amux-out)
    (ALU Amux-out B-Bus MIR:ALU ALU-out N Z)
    (MicroSeqLogic N Z MIR:COND MicroSeqLogic-out)
    (Mux/N MPC-Inc-out MIR:ADDR MicroSeqLogic-out Mmux-out)
    (Decoder/N MIR:SH (list GROUND Shifter-Right? Shifter-Left? GROUND))
    (Shifter/N Shifter-Left? Shifter-Right? ALU-out C-Bus)
    (And MIR:MBR Clock:4 MBR?)
    (Latch/N MBR? C-Bus MBR)
    (And Clock:4 MIR:ENC Write-C?)
    (RegisterSet Write-C? C-Bus Csel Registers)
    (Latch/N Clock:4 Mmux-out MPC-out)
    (Increment/N MPC-out MPC-Inc-carry MPC-Inc-out)))

```



```
(define (simulate! net)
  (for ([n (in-list net)])
    (match-define (nand a b o) n)
    (box-set! o
              (not
               (and (unbox a)
                    (unbox b))))))
```



```
typedef uint64_t wire_t;  
wire_t WIRES[111] = {0};  
typedef uint8_t wireidx_t;
```



```

static void nand(wireidx_t aA, uint8_t aB,
                wireidx_t bA, uint8_t bB,
                wireidx_t oA, uint8_t oB) {
    uint8_t L = (WIRES[aA] & ((wire_t)1<<aB)) ? 1 : 0;
    uint8_t R = (WIRES[bA] & ((wire_t)1<<bB)) ? 1 : 0;
    uint8_t A = L & R ? 0 : 1;
    wire_t O = WIRES[oA];
    wire_t M = ((wire_t)1<<oB);
    WIRES[oA] = A ? (O | M) : (O & (~M));
}

```



```
void cycle() {
    nand(47, 49, 47, 49, 47, 50);
    nand(47, 49, 47, 49, 47, 51);
    nand(47, 51, 47, 51, 47, 52);
    nand(47, 53, 47, 53, 47, 54);
    nand(47, 53, 47, 53, 47, 55);
    nand(47, 55, 47, 55, 47, 56);
    nand(47, 50, 47, 54, 47, 57);
    nand(47, 57, 47, 57, 47, 58);
    nand(47, 50, 47, 56, 47, 59);
    nand(47, 59, 47, 59, 47, 60);
    nand(47, 52, 47, 54, 47, 61);
    nand(47, 61, 47, 61, 47, 62);
    nand(47, 52, 47, 56, 47, 63);
    nand(47, 63, 47, 63, 48, 0);
    ... 7000 more lines
    nand(0, 6, 47, 39, 47, 40);
    nand(47, 39, 47, 38, 47, 41);
    nand(47, 40, 47, 41, 24, 40);
    nand(0, 6, 47, 38, 47, 42);
    nand(47, 42, 47, 42, 47, 43);
    nand(0, 7, 47, 43, 47, 44);
    nand(0, 7, 47, 44, 47, 45);
    nand(47, 44, 47, 43, 47, 46);
    nand(47, 45, 47, 46, 24, 49);
    nand(0, 7, 47, 43, 47, 47);
    nand(47, 47, 47, 47, 47, 48); }
```



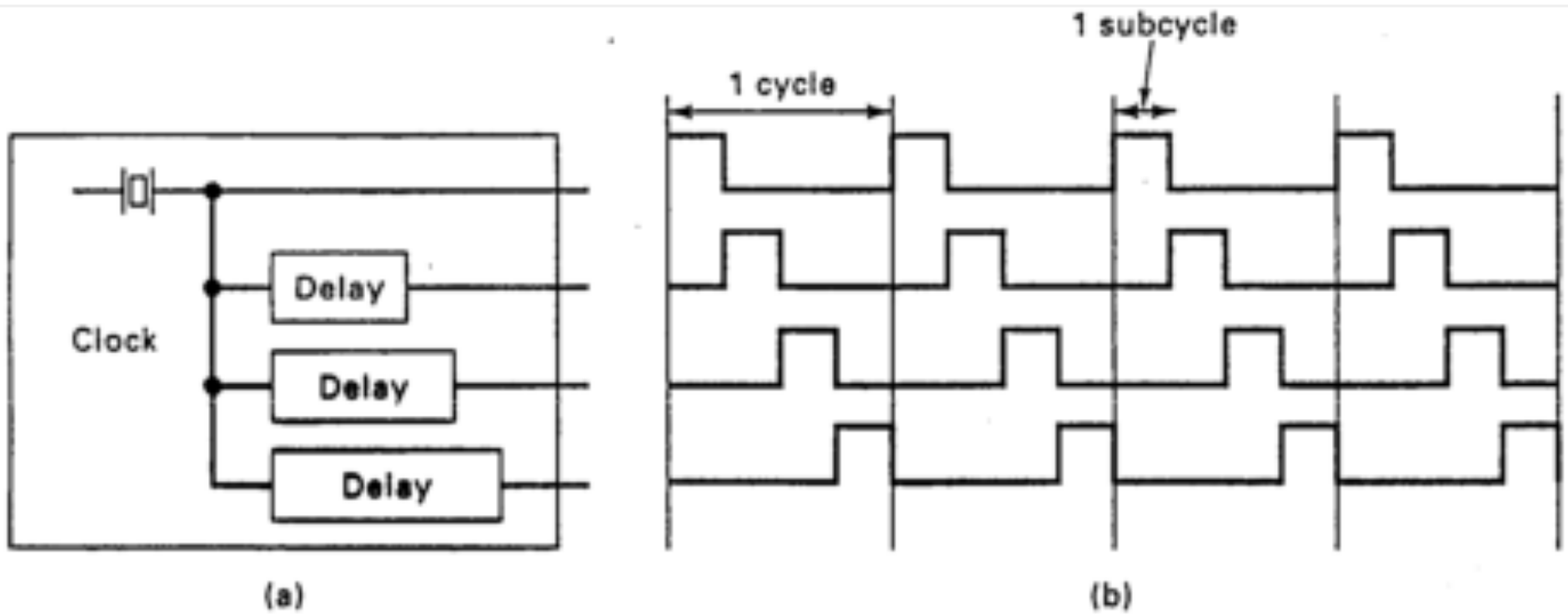


Fig. 4-5. (a) A clock with four outputs. (b) The output timing diagram.

